
## 2280 AZ Solutions


i) The instruction BRz DONE is using the condition codes of ADD R3, R3, R3 instead of ADD R2, R7, #-1

Switching the 2 instructions fixes the problem.

3) a) 
$$X = 0 \implies S = A + B$$
 (or vice versa)  $X = 1 \implies S = A + C$ 

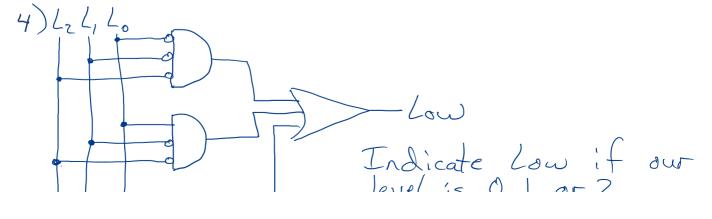b) The circuit stays the same, we just change the inputs to perform 2's comp for subtraction



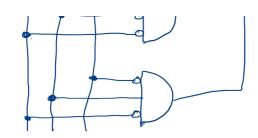

Indicate Low it our level is 0, 1, or 2.

5) time event 1: when A=B=C=1, Q is held (R=S=1). Q can be 0 or 1 (your choice) time event 7:  $C \rightarrow 0$ , Q is held. time event 3:  $A,B \rightarrow 0$ ,  $C \rightarrow 1$ reset Q (R=0,S=1)

time event 4: A>1, C>0 set Q (R=1, S=0)

timing diagram: Cassuming Q=1 to start)

time >